

96
ELECTRONICS TECHNICIAN

Name AGUSTIN LUCAS
Date Jan-30-57

Final Examination--1st Semester

The following problems are multiple choice. Select the correct answer by placing its letter in the space provided.

1. C Increasing the temperature of most metals will:
a. not affect the resistance.
X B increase the resistance.
x c. decrease the resistance.
2. C In a series circuit:
a. more current flows through the resistor near the B plus.
b. " " " " " " " negative.
X c. the same current flows in each resistor.
d. none of the above.
3. a The resultant resistance of a parallel circuit:
X a. is equal to the applied voltage divided by the applied current.
b. varies with the applied voltage.
c. varies with the line current.
4. d The total resistance of a parallel circuit:
a. decreases if the resistance of any branch increases.
b. remains the same if the resistance of any branch changes.
c. increases if the resistance of any branch decreases.
X d. increases if the resistance of any branch increases.
5. b Electrical work is done when:
a. watts.
b. electrons .
c. volts
are forced along a wire.
6. a One half of a cycle is called:
X a. an alternation.
b. a harmonia.
c. the frequency.
d. the phase.
7. C The r.m.s. value of a sine wave of alternating current is the same as the:
a. peak value.
b. max. value.
X c. effective value.
d. average value.
8. C The effective value of an alternating sine-wave current or voltage is equal to:
a. .318
b. 1.414 times the max. value.
X c. .707
d. .636
9. b When a body has electrons removed from it, it is said to be:
a. negatively charged.
X b. positively " .
c. neutral.

THE JOURNAL OF THE

AMERICAN MEDICAL ASSOCIATION

PUBLISHED WEEKLY

CHICAGO, ILL., U.S.A.

VOLUME 10

NUMBER 1

JANUARY, 1917

PRICE, FIVE CENTS

Subscription price, \$5.00 per annum in advance

Single copies, 15 cents

Entered as second-class matter, June 26, 1902

Postage paid at Chicago, Ill.

Acceptance for mailing at special rate of postage provided for in Act of October 3, 1917

Authorizes sale at special rate of postage provided for in Act of October 3, 1917

Postmaster: This publication is published weekly except on Sundays and holidays

Copyright, 1917, by American Medical Association

Printed at the Chicago Press, Chicago, Ill.

Published by the American Medical Association, 535 North Dearborn Street, Chicago, Ill.

Subscription orders, notices of change of address, and other correspondence should be sent to the Editor, American Medical Association, 535 North Dearborn Street, Chicago, Ill.

Claims for missing issues will only be considered if made immediately on receipt of subsequent issue

Second-class postage paid at Chicago, Ill.

Postage paid at Chicago, Ill.

Postage paid at Chicago, Ill.

Postage paid at Chicago, Ill.

Postage paid at Chicago, Ill.

Postage paid at Chicago, Ill.

Postage paid at Chicago, Ill.

Postage paid at Chicago, Ill.

Postage paid at Chicago, Ill.

Postage paid at Chicago, Ill.

Postage paid at Chicago, Ill.

10. a The time constant of a capacitive circuit is given by the formula:

- ☒ a. $T = RC$
- b. $T = C/R$
- c. $T = R/C$

11. a When capacitors are connected in parallel the total capacitance is always:

- ☒ a. greater than the capacitance of the smallest capacitor.
- b. less than
- c. equal to

12. a When current flows in the secondary of a transformer it will set up a flux that will act in:

- ☒ a. the opposite direction.
 - b. the same direction.
- as the flux set up by the current in the primary.

13. c For the following problems refer to fig. 1

With a signal applied to the input of V-1, if capacitor C-1 were removed from the circuit:

- a. the gain of the amplifier would increase.
- b. the amplifier would oscillate.
- ☒ c. the gain of the amplifier would decrease.
- d. No real difference in output would be apparent.

14. b C-2 shorted:

- a. the tube could be damaged by excessive plate current.
- ☒ b. the screen dropping resistor could be damaged.
- c. the gain of the amplifier would increase at high freq.
- d. the gain of the amplifier would increase at low freq.

15. c With R-3 open the voltage at the plate of V-2 would be:

- a. 180 volts.
- b. ~~0~~ 0 volts.
- ☒ c. 300 volts.
- d. none of the above.

16. b A tube operating as a class B amplifier is biased at:

- a. about midpoint of the characteristic curve.
- ☒ b. about cut-off.
- c. about 2 to 3 times cut-off.
- d. about 0 volts.

17. b A single-ended class A power amplifier, as compared to other classes of power amplifiers, such as AB and B_p produces:

- a. high distortion and low power.
- ☒ b. low distortion and low power.
- c. high distortion and high power.
- d. low distortion and high power.



18. d For the following refer to fig. 2.

If the output, or B plus voltage were measured and found to be somewhat higher than normal, which of the following could cause this condition:

- a. C-1 open.
- b. L open.
- c. C-2 shorted.
- ☒ d. R open

19. d B plus lower than normal:

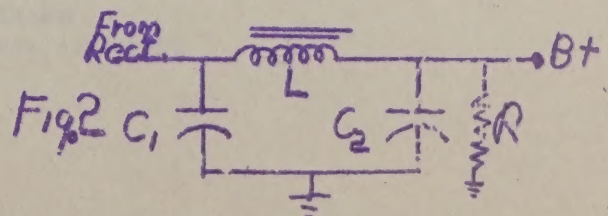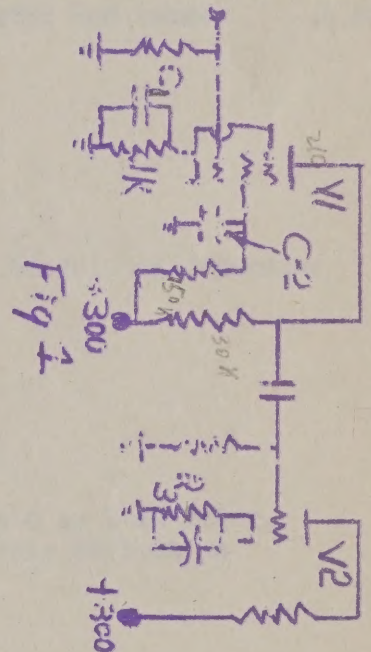
- a. L shorted.
- b. L open
- c. R open
- ☒ d. C-2 leaky



...the ... of the ...
 ...the ... of the ...
 ...the ... of the ...

...the ... of the ...
 ...the ... of the ...

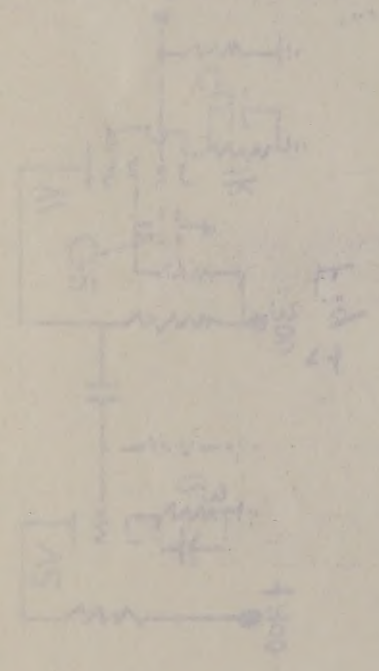...the ... of the ...
 ...the ... of the ...




...the ... of the ...
 ...the ... of the ...

...the ... of the ...
 ...the ... of the ...

...the ... of the ...
 ...the ... of the ...

...the ... of the ...
 ...the ... of the ...

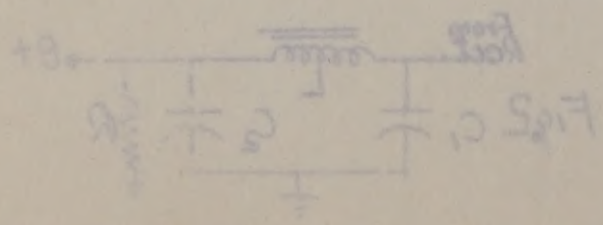...the ... of the ...
 ...the ... of the ...



...the ... of the ...
 ...the ... of the ...

20. b If the voltage applied to a circuit is doubled and the resistance of the circuit is tripled, the new value of current will be:
- a. The same
 - ☒ b. $2/3$ as great
 - c. $3/4$ as great
 - d. Twice as great
 - e. $1/2$ as great
21. b If resistors of 5, 3, and 15 ohms are connected in parallel, what will their total resistance be?
- a. 23 ohms
 - ☒ b. 1.66 ohms
 - ☒ c. .166 ohms
 - d. 16.6 ohms
 - e. 8 ohms.
22. b When a 25 ohm 0 to 1 Ma meter is shunted by a 4 ohm resistor and reads .4 ma the total current through the shunt meter is:
- a. .4 ampe
 - ☒ b. 2.9 ma
 - ☒ c. 2.5 ma
 - d. 30 ma
 - e. .04 ma
23. F If two voltmeters are connected in series, how would you be able to determine the total voltage drop across both instruments?
- a. Multiply the two readings
 - ☒ b. Subtract one reading from another
 - d. Square the two readings
 - e. Add the two readings
 - ☒ f. Take the square of the sum of the two readings
24. a What exact value of series resistor should be used with a 0 to 1 ma meter, having an internal resistance of 27 ohms to get a full scale deflection of 70 volts?
- ☒ a. 69,973 ohms
 - b. 33,432 ohms
 - c. 74,999 ohms
 - d. 71.000 ohms.
25. C The suppressor grid in a pentode will:
- a. Prevent secondary emission from occurring
 - b. reduce plate current flow
 - ☒ c. Reduce the harmful effects of secondary emission
 - d. Cause an increase in screen current flow
26. C What feature of a remote cut-off pentode distinguishes it from a sharp cut-off pentode?
- a. The plate structure is closer to the cathode
 - b. The screen grid is closer to the cathode
 - ☒ c. The manner in which the grid structure is built
 - d. No suppressor is used

The voltage applied to a circuit is doubled and the resistance of the circuit is halved. The new value of current will be:

- a. 2 times
- b. 1/2 times
- c. 4 times
- d. 1/4 times

Resistors of 5, 10, and 15 ohms are connected in parallel. What will be the total resistance?

- a. 3 ohms
- b. 1/3 ohms
- c. 15 ohms
- d. 30 ohms

When a 25 ohm 0 to 1 mA meter is shunted by a 1 ohm resistor and reads 0.5 mA, what current flows through the shunt resistor?

- a. 1 mA
- b. 2 mA
- c. 0.5 mA
- d. 0.25 mA

Two voltmeters are connected in series. The first meter has a full scale deflection of 100 V and the second has a full scale deflection of 50 V. What is the total voltage drop across both instruments?

- a. 150 V
- b. 100 V
- c. 50 V
- d. 25 V

What value of series resistor should be used with a 0 to 1 mA meter having an internal resistance of 50 ohms to give a full scale deflection of 10 volts?

- a. 1000 ohms
- b. 100 ohms
- c. 10 ohms
- d. 1 ohm

The voltage across a resistor is 10 V and the current through it is 2 mA. What is the power dissipated in the resistor?

- a. 20 mW
- b. 2 mW
- c. 0.2 mW
- d. 0.02 mW

What is the value of a resistor if a 10 V source is connected in series with it and the current through it is 2 mA?

- a. 5 ohms
- b. 10 ohms
- c. 20 ohms
- d. 50 ohms

27. b The E_p - I_p characteristic curve of a triode has a knee, or bend, at the start of the curve. This is caused by the effects of:
- The heater or filament
 - ☒ b. The space charge
 - The interelectrode capacitance
 - Transit time

The following statements are either True or False--Circle the correct letter preceding the statement.

- T ☒ F 1. The average DC output voltage of a choke input filter is higher than a condenser input.
- ☒ T F 2. Space charge could be overcome by increasing E_p .
- T ☒ F 3. Most receivers use a resistor in place of a filter choke because a higher output voltage is possible.
- ☒ T F 4. The output of a full-wave rectifier is easier to filter than the output of a half rectifier.
- ☒ T F 5. A non-synchronous vibrator supply requires a rectifier tube.
- ☒ T F 6. A dynamic characteristic is made with conditions similar to actual operating conditions.
- ☒ T F 7. Vacuum tubes conduct current in only one direction.
- ☒ T F 8. An ampere is a rate of flow of electrons.
- T ☒ F 9. A one thousand ohm per voltmeter requires 100 ma for full scale deflection.
- T ☒ F 10. If the shunt of an ammeter is accidentally disconnected from a circuit the pointer will return to zero.

Electronics--Final Exam.--1st Semester, Con't.

28. In electricity, the rate of its doing work is called POWER and the unit is WATT.
29. The total current in a parallel circuit is equal to THE SUM OF THE CURRENT IN EACH BRANCH.
30. Conductance is the RECIPROCAL of the resistance.
31. Flux is the LINES OF FORCE of a magnetic FIELD.
32. Energy is stored in the DIELECTRIC of a capacitor and in an inductance in the MAGNETIC FIELD (LEMF).
33. A one thousand ohm per voltmeter requires ONE (1) ma. for full scale deflection.
34. 60-40 solder means 60% TIN and 40% LEAD.
35. c The suppressor grid in a pentode will:
- a. Prevent secondary emission from occurring.
 - b. Reduce plate current flow.
 - ☒ c. Reduce the harmful effects of secondary emission.
 - d. Cause an increase in screen current flow.
36. c What feature of a remote cut-off pentode distinguishes it from a sharp cut-off pentode?
- a. The plate structure is closer to the cathode.
 - b. The screen grid is closer to the cathode.
 - ☒ c. The manner in which the grid structure is built.
 - d. No suppressor is used.
37. b The Ep-Ip characteristic curve of a triode has a knee, or bend, at the start of the curve. This is caused by the effects of:
- a. The heater or filament.
 - ☒ b. The space charge.
 - c. The interelectrode capacitance.
 - d. Transit time.

For V-1 of Fig. 1, values are as follows:

Plate load resistor	30K
Screen resistor	150K ✓
Bias resistor	1K

Plate voltage (No Sig.)	210 Volts
Bias	3.8 Volts
Input Signal	.1 volt peak to peak

The sharp characteristic curve of a triode has a knee, or bend, at the start of the curve. This is caused by the effects of:

1. The heater or filament.
2. The space charge.
3. The cathode-cathode capacitance.
4. The control grid.

For 4-5 of Fig. 1, values are as follows:

10K	Plate load resistor
150K	Control grid resistor
1K	Screen grid resistor

Wave voltage (No. 210) Voice
 3.5 Voice
 1 volt peak to peak

The following two problems are worth 3 points each.

Referring to figure 1, calculate the value of screen voltage on V-1 when no signal is applied to the grid. 180 VOLTS

39. Referring to figure 1, when the input signal shown is applied to the grid of V-1, the plate current increases by .1 ma on the maximum positive swing of the signal, and decreases by .1 ma on the negative swing of the signal. Calculate the gain of amplifier V-1. 60 GAIN

THE UNIVERSITY OF CHICAGO PRESS

THE UNIVERSITY OF CHICAGO PRESS

THE UNIVERSITY OF CHICAGO PRESS

U